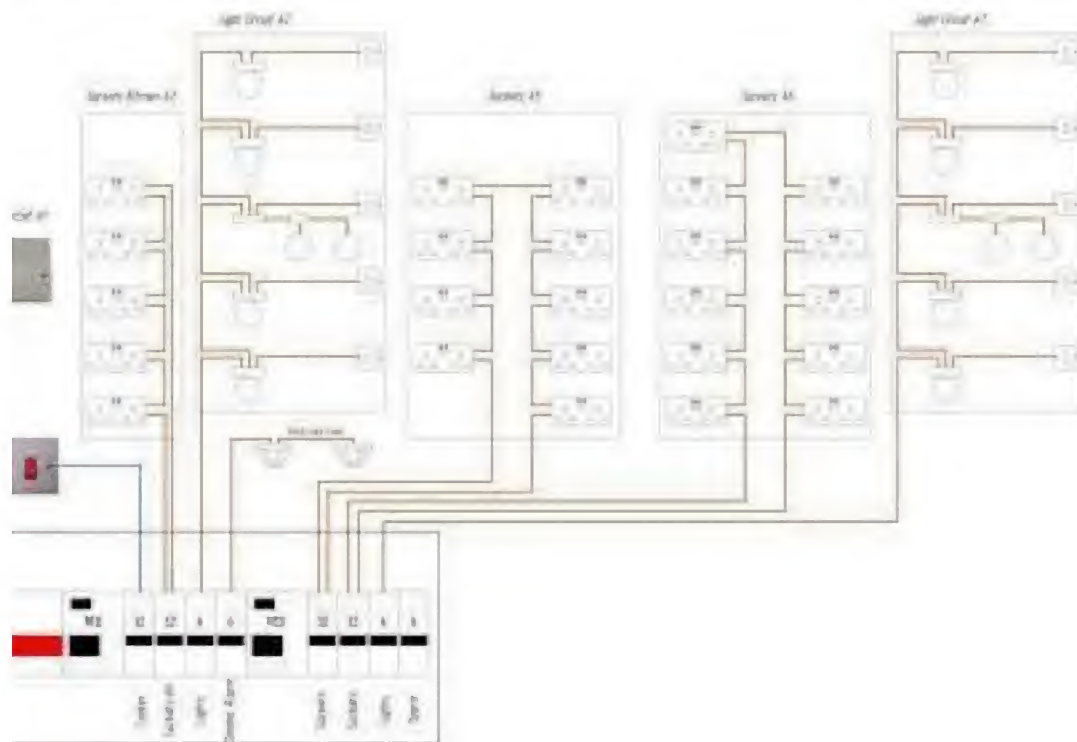



Wiring Circuit Diagram



**A.K** AK Engineers  
Presents

## Electrical wiring tutorial Part 3



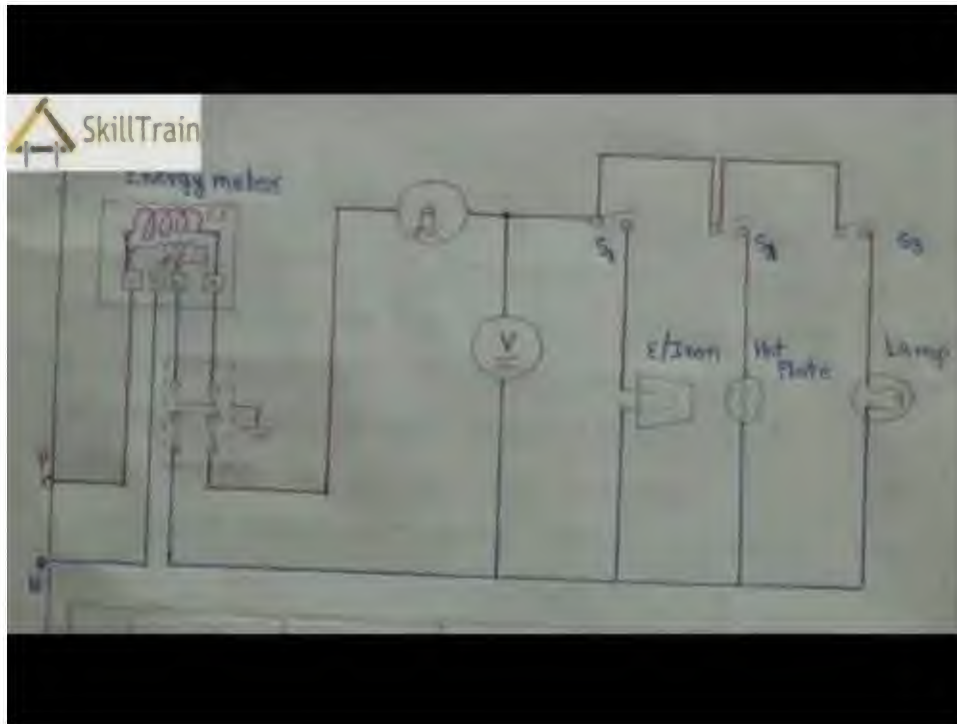


# घर की वायरिंग

[www.electguru.com](http://www.electguru.com)




करवाते समय  
ध्यान रखने  
वाली बातें

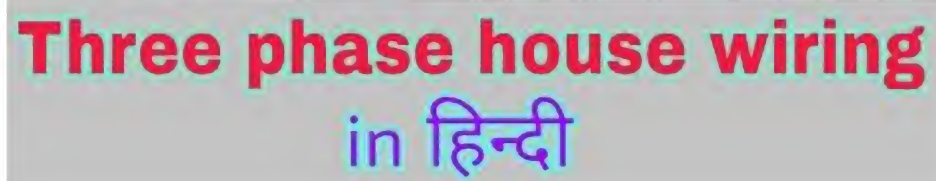

— 2.5mm cable  
— 4mm cable

# Wiring Diagram of Breaker Box

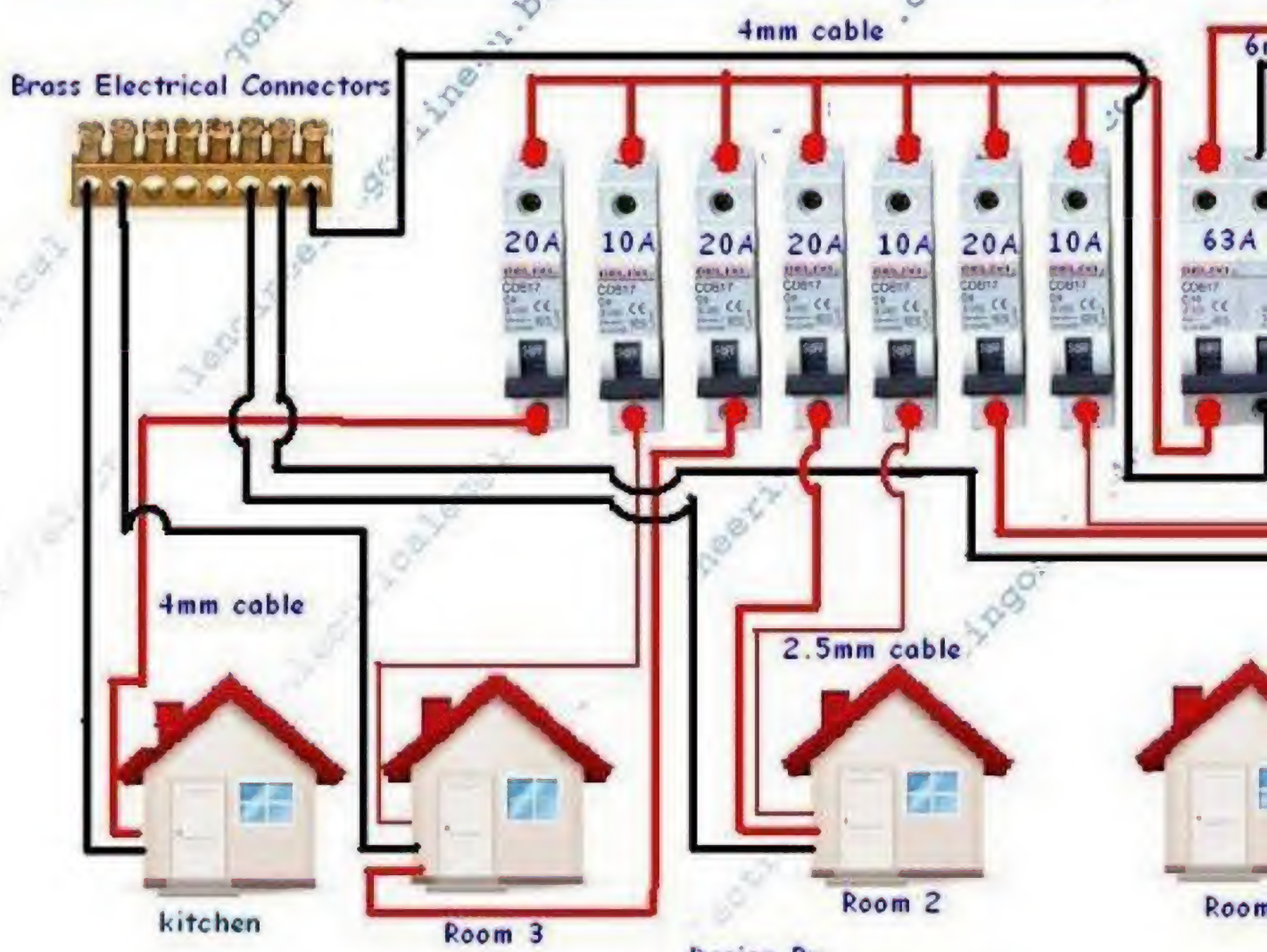

Design By  
Sikandar Haidar